

# ELC 2137 Lab 10: 7-segment Display with Time-Division Multiplexing

Alexander Noll

April 14, 2020

## Summary

Building upon previous labs, we utilized registers and sequential logic to design timers. Using these timers, the calculator and 7-segment display driver were combined to create a 4 digit calculator with display.

## Q&A

1. The three main groups of the RTL definition of sequential logic include state memory, next-state, and output logic. 2. 3.  $Q_{next} = Q_{reg}[N-2], 1$ .

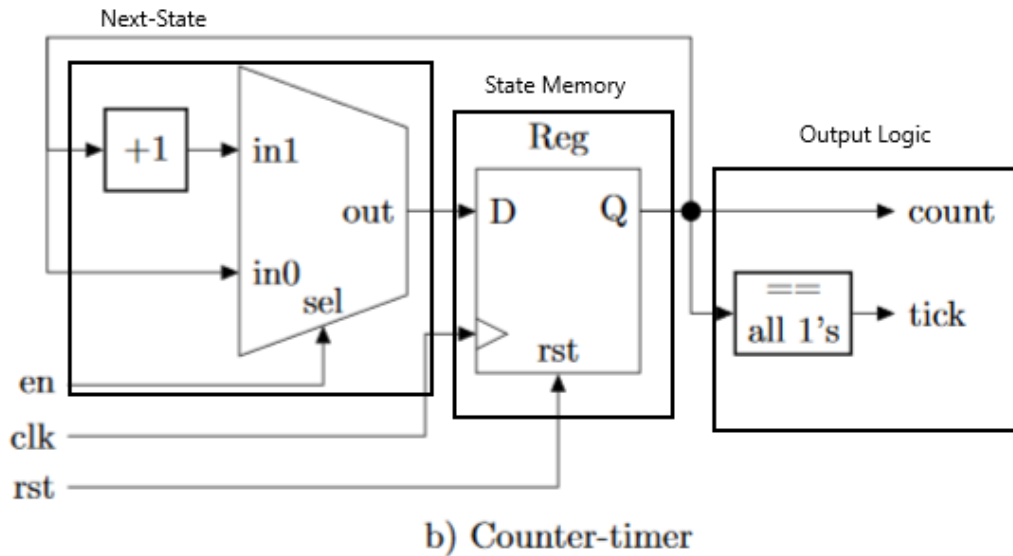


Figure 1: RTL Groups in a Counter Timer

## Results

Table 1: *register* expected results table

Time (ns):	0-1	1-2	2-3	3-4	4-5	5-6	6-7	7-8	8-9	9-10	10-11	11-12	12-13	13-14	14-15
clk	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0
en	0	0	0	0	0	0	1	1	1	1	1	1	0	0	0
rst	0	0	0	1	1	1	0	0	0	0	0	0	0	0	0
Q (dec)	X	X	X	0	0	0	0	1	1	2	2	3	3	3	3
tick	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

 


Figure 2: Counter Test Waveform

Table 2: *alu* expected results table skeleton

Clock Cycles:	0-1	1-2	2-3	3-4	4-5	5-6	6-7	7-8	8-9	9-10	10-11	11-12	12-13	13-14	14-15
Input	49	49	49	49	49	49	49	49	49	49	49	49	49	49	49
Reset	0	0	0	0	0	1	1	1	1	1	0	0	0	0	0
Seg	40	40	40	40	40	30	30	30	30	30	78	40	40	30	78
an	X	X	X	X	X	e	e	e	e	e	d	b	7	e	d
dp	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1

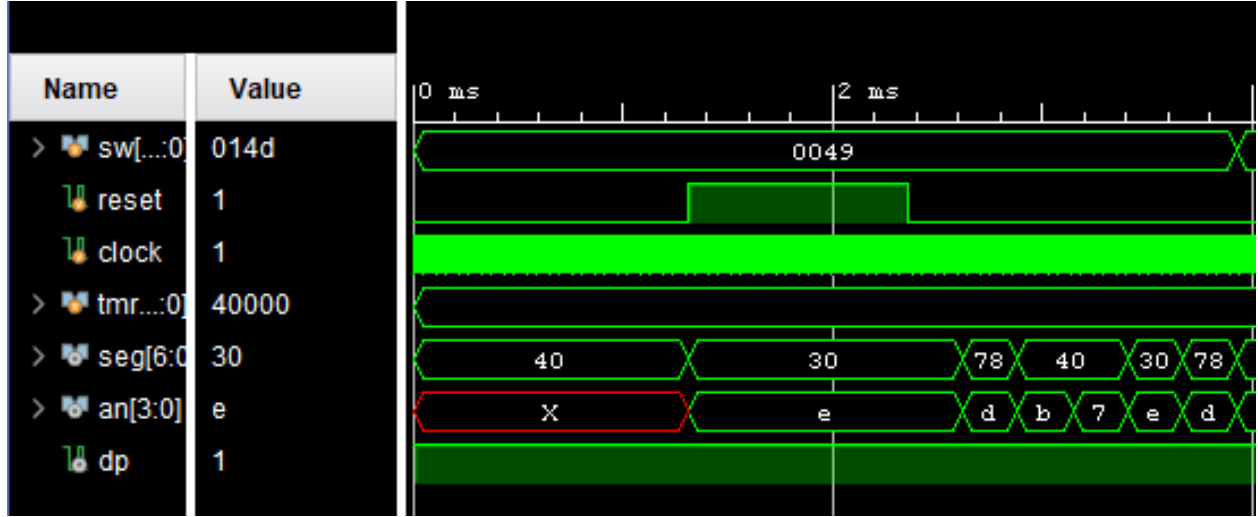


Figure 3: 7-Segment Driver Test Waveform

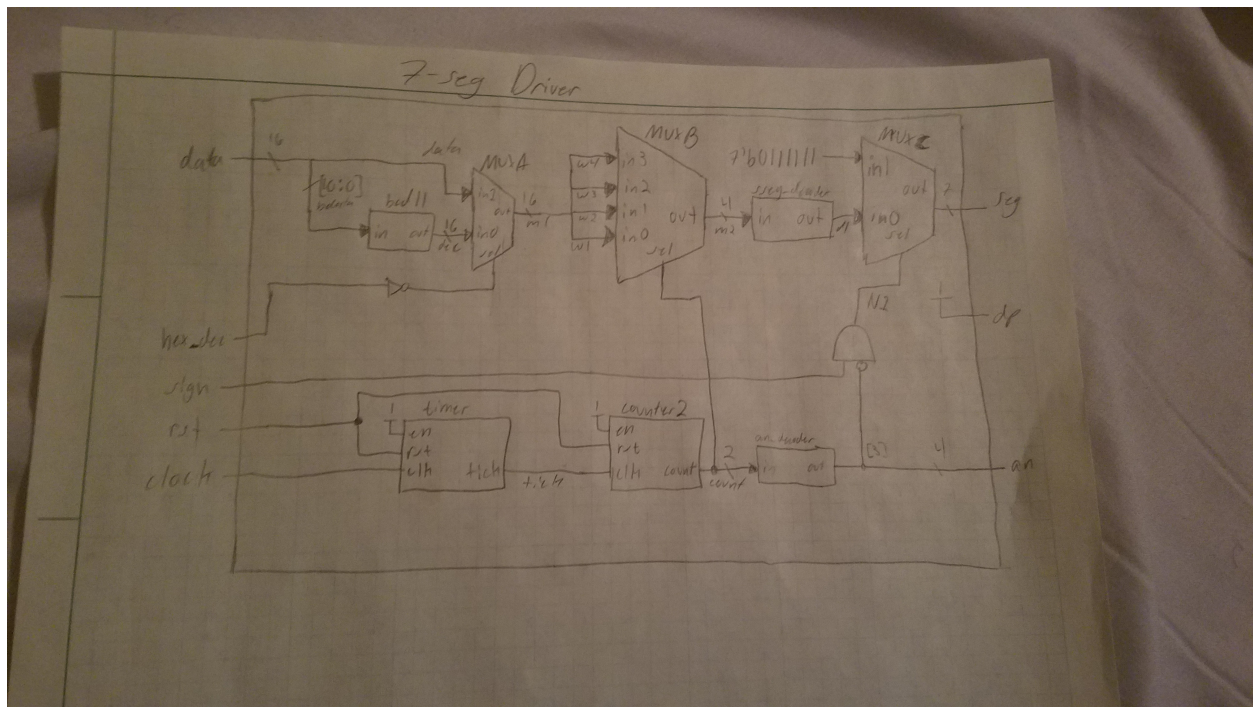


Figure 4: Sseg4 TDM Schematic Drawing

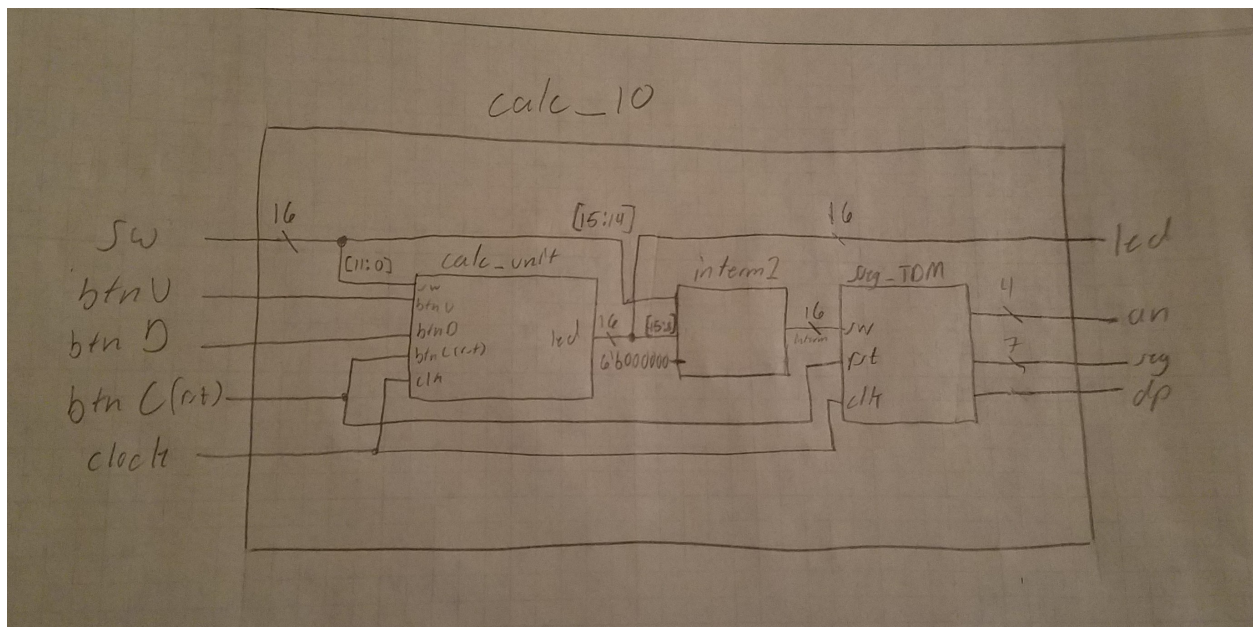


Figure 5: Calc Lab10 Schematic Drawing

## Code

Listing 1: Verilog Counter Source

---

```
module counter#( parameter N=1)
(
input clk , rst , en ,
output [N -1:0] count ,
output tick
);
// internal signals
reg [N -1:0] Q_reg , Q_next;
// register (state memory)
always @(posedge clk , posedge rst)
begin
if (rst)
Q_reg <= 0;
else
Q_reg <= Q_next;
end
// next -state logic
always @*
begin
if (en)
Q_next = Q_reg + 1;
else
Q_next = Q_reg;
end
// output logic
assign count = Q_reg;
assign tick = (Q_reg =={N{1'b1}}) ? 1'b1 : 1'b0;
endmodule
```

---

Listing 2: Verilog Sseg Source

---

```
module sseg_TDM(
input [15:0] sw,
input reset, clock,
output [3:0] an,
output [6:0] seg,
output dp);
reg [15:0] data;
reg hex_dec,sign;
reg [10:0] bdata;
wire [15:0] dec;
wire [15:0] m1;
wire [3:0] m2;
wire [6:0] d1;
wire N1;
wire [3:0] w1, w2, w3, w4;
wire [1:0] count;
wire [17:0] Q;
wire t,tick;

assign data = {4'b0000, sw[11:0]};
```

---

```

assign w1 = m1[3:0];
assign w2 = m1[7:4];
assign w3 = m1[11:8];
assign w4 = m1[15:12];
assign N1 = {sign & (~an[3])};
assign dp = 1;
assign bdata = sw[10:0];
assign sign = sw[14];
assign hex_dec = sw[15];

BCD11 BCD(.number(bdata), .nout(dec));

mux2 #(.N(16)) MUXA(.in0(data), .in1(dec), .sel(hex_dec), .out(m1));

counter #(.N(19)) timer (.clk(clock), .en(dp), .rst(reset), .count(Q)
, .tick(tick));

counter #(.N(2)) counter2 (.clk(tick), .en(dp), .rst(reset), .count(
count), .tick(t));

mux4 #(.N(4)) MUXB(.in0(w1), .in1(w2), .in2(w3), .in3(w4), .dig_sel(
count), .out(m2));

an_decode AN1(.dig_sel(count), .an(an));

sseg_decoder SSEG1(.num(m2), .sseg(d1));

mux2 #(.N(7)) MUXC(.in0(d1), .in1(7'b0111111), .sel(N1), .out(seg));

endmodule

```

---

Listing 3: Verilog Top Lab 10 Source

```

module calc_lab10(
    input [15:0] sw,
    input btnU, btnD, btnC, reg clk,
    output [3:0] an,
    output [6:0] seg,
    output dp,
    output [15:0] led
);

    wire [15:0] interm1;

    top_lab9 calc_unit (.sw(sw[11:0]), .btnU(btnU), .btnD(btnD), .btnC(btnC), .clk
(clk), .led(led));

    assign interm1={sw[15:14], 6'b000000, led[15:8]};

    sseg_TDM disp_unit (.sw(interm1), .reset(btnC), .clock(clk), .an(an), .seg(seg
), .dp(dp));

```

```
endmodule
```

---

Listing 4: Verilog Sseg Test Bench

---

```
module sseg_TDM_test();
reg [15:0] sw;
reg reset, clock;
reg [18:0] tmrcyc;
wire [6:0] seg;
wire [3:0] an;
wire dp;

assign tmrcyc= 19'b10000000000000000000;
sseg_TDM Disp (.sw(sw),.reset(reset),.clock(clock),.seg(seg),.an(an),.dp(
    dp));

    always begin
        clock = ~clock; #(0.5);
    end

    initial begin
        clock=0; sw=16'b000000001001001; reset =0; #(5*tmrcyc);
        reset = 1; #(4*tmrcyc);
        reset = 0; #(6*tmrcyc);
        sw=16'b000000001011001;          #(4*tmrcyc);
        sw=16'b000000011001101;          #(6*tmrcyc);
        sw=16'b000000001100111;          #(4*tmrcyc);
        reset = 0; #(6*tmrcyc);
        reset = 1; #(4*tmrcyc);
        sw=16'b000000101001101;          #(4*tmrcyc);
        $finish;
    end
end

endmodule
```

---

Listing 5: Verilog Counter Test Bench

---

```
module counter_test();
    reg clk , en , rst;
    wire [17:0] Q;
    wire tick;
    counter #(N(18)) r (.clk(clk),
        .en(en), .rst(rst), .count(Q), .tick(tick));

    always begin
        clk = ~clk; #(0.5);
    end

    initial begin
        clk=0; en=0; rst =0; #3;
        rst = 1; #3;
        en = 1; rst = 0; #6;
        en = 0;          #3;
        en = 1;          #6;
        en = 0;          #3;
        en = 1;          #(19'b10000000000000000001);
        $finish;
    end
endmodule
```

---